 


THM - University of Applied Sciences  
Faculty IEM



# HC1 Central Processing Unit

VHDL Design

**Author:** Matthias Röhl  
matthias.roell@iem.thm.de

**Date:** December 2014

# Inhaltsverzeichnis

<b>I</b>	<b>Abbildungsverzeichnis</b>	<b>III</b>
<b>II</b>	<b>Tabellenverzeichnis</b>	<b>III</b>
<b>III</b>	<b>Abkürzungsverzeichnis</b>	<b>III</b>
<b>1</b>	<b>HC1 Architecture &amp; Overview</b>	<b>1</b>
1.1	Block & RTL Diagram . . . . .	1
1.2	Instruction Set . . . . .	2
1.2.1	Befehle . . . . .	3
1.3	Default Program & Simulation . . . . .	3
1.4	Modifikationen . . . . .	4
<b>2</b>	<b>Entities</b>	<b>5</b>
2.1	Accumulator . . . . .	5
2.1.1	Ports . . . . .	5
2.2	Arithmetic Logical Unit . . . . .	6
2.2.1	Ports . . . . .	6
2.3	Control Unit . . . . .	7
2.3.1	Ports . . . . .	7
2.3.2	State Machine . . . . .	7
2.3.3	Implementationshinweis . . . . .	9
2.4	Instruction Register . . . . .	11
2.4.1	Ports . . . . .	11
2.5	Memory Unit . . . . .	12
2.5.1	Ports . . . . .	12
2.6	Program Counter . . . . .	13
2.6.1	Ports . . . . .	13
2.7	Central Processing Unit . . . . .	14
2.7.1	Ports . . . . .	14
2.7.2	Mapping . . . . .	14
2.8	Cyclone II Pin Mapping - HC1 . . . . .	15
<b>A</b>	<b>Appendix</b>	<b>i</b>
A.1	Accumulator - VHDL . . . . .	i
A.2	Arithmetic Logical Unit - VHDL . . . . .	iii
A.3	Control Unit - VHDL . . . . .	iv
A.4	Instruction Register - VHDL . . . . .	xiv
A.5	Memory Unit - VHDL . . . . .	xv
A.6	Program Counter - VHDL . . . . .	xvii
A.7	CPU - VHDL . . . . .	xix

## I Abbildungsverzeichnis

Abb.: 1	HC1 Architektur Diagramm . . . . .	1
Abb.: 2	RTL Diagramm . . . . .	2
Abb.: 3	Program Simulation . . . . .	3
Abb.: 4	Accumulator Unit - Block . . . . .	5
Abb.: 5	Arithmetic Logical Unit - Block . . . . .	6
Abb.: 6	Control Unit - Block . . . . .	7
Abb.: 7	Control Unit - State Machine . . . . .	8
Abb.: 8	Instruction Register - Block . . . . .	11
Abb.: 9	Memory Unit - Block . . . . .	12
Abb.: 10	Program Counter - Block . . . . .	13
Abb.: 11	Central Processing Unit - Block . . . . .	14

## II Tabellenverzeichnis

Tab.: 1	Instruction Set . . . . .	2
Tab.: 2	Accumulator Ports . . . . .	5
Tab.: 3	Arithmetic Logical Unit Ports . . . . .	6
Tab.: 4	Control Unit Input Ports . . . . .	7
Tab.: 5	Control Unit Output Ports . . . . .	8
Tab.: 6	Instruction Register Ports . . . . .	11
Tab.: 7	Memory Unit Ports . . . . .	12
Tab.: 8	Program Counter Ports . . . . .	13
Tab.: 9	Central Processing Unit Ports . . . . .	14

## III Abkürzungsverzeichnis

# 1 HC1 Architecture & Overview

Die HC1 CPU ist ein simpler 8 Bit Rechner. Er ist fähig 10 verschiedene Operationen durchzuführen und stellt einen 32 Byte Speicher zur Verfügung.

## 1.1 Block & RTL Diagram

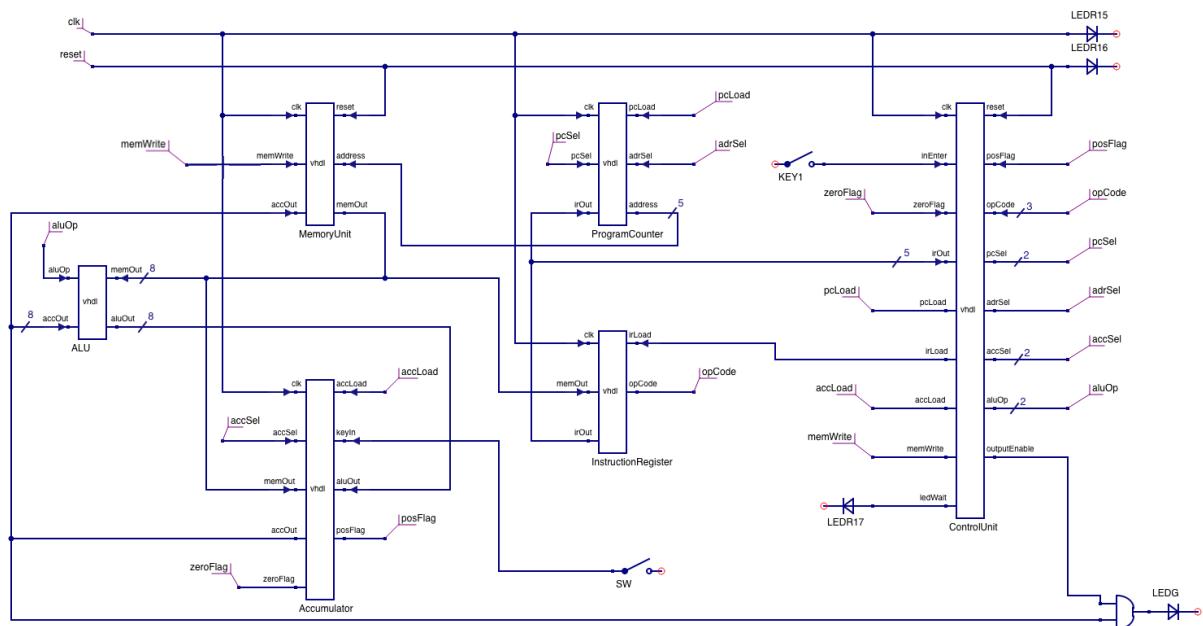


Abbildung 1: HC1 Architektur Diagramm

Das Diagramm zeigt die Bausteine des HC1 Rechners. Diese werden durch eine CPU Entität über Signale verknüpft.

Die CPU besteht aus den folgenden Bausteinen:

- Accumulator
- Arithmetic Logical Unit (ALU)
- Control Unit
- Instruction Register
- Memory Unit
- Program Counter

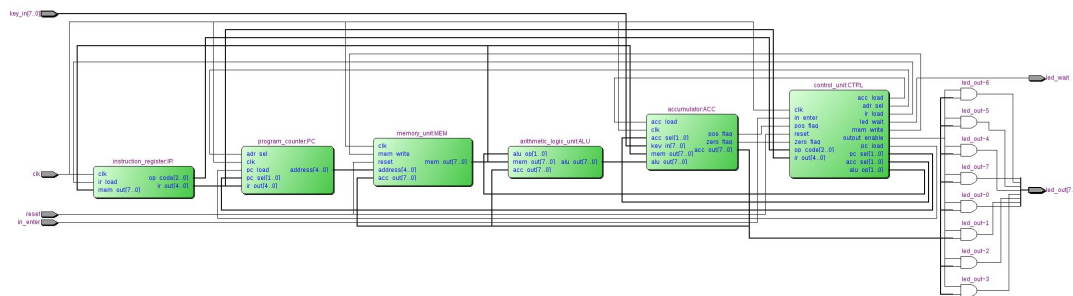


Abbildung 2: RTL Diagramm

## 1.2 Instruction Set

Der Befehlssatz des Rechner besteht aus 10 verschiedenen Instruktionen.

Jeder Befehl enthält hierbei 3 Op-Code Bits und 5 Adress Bits.

Befehl	OpCode	Data	Taktzyklen
LOAD	000	aaaaa	5
STORE	001	aaaaa	5
ADD	010	aaaaa	5
SUB	011	aaaaa	5
NAND	100	eeeeee	5
IN	100	00000	5
OUT	100	00001	5
JZ	101	aaaaa	4
JPOS	110	aaaaa	4
J	111	aaaaa	4

Tabelle 1: Instruction Set

### Taktzyklen:

Die dargestellte Takzyklenanzahl der Befehle kann zwischen verschiedenen Implementa-  
tionen abweichen.

Daten:

Die angegebene Datenkodierung stellt folgende Werte dar:

1. aaaaa - Adresse im Bereich 0 - 32
2. eeeee - Adresse im Bereich 2 - 32

### 1.2.1 Befehle

Folgend eine kurze Funktionsbeschreibung der Befehle:

**LOAD** Lädt einen Wert aus dem Hauptspeicher in den Akkumulator.

**STORE** Speichert einen Wert aus dem Akkumulator in den Hauptspeicher.

**ADD** Addiert einen Wert aus dem Hauptspeicher zu dem Wert im Akkumulator.

**SUB** Subtrahiert einen Wert aus dem Hauptspeicher von dem Wert im Akkumulator.

**NAND** Führt eine NAND Operation mit dem Wert im Hauptspeicher und dem Akkumulatorwert durch.

**IN** Speichert eine Eingabe im Akkumulator.

**OUT** Setzt den aktuellen Akkumulatorwert auf den Ausgangsbus.

**JZ** Führt eine Sprunganweisung durch, wenn der Akkumulatorinhalt gleich 0 ist (zero-Flag).

**JPOS** Führt eine Sprunganweisung durch, wenn der Akkumulatorinhalt größer 0 ist (posFlag).

**J** Führt eine Sprunganweisung durch..

## 1.3 Default Program & Simulation

 


Abbildung 3: Program Simulation

## 1.4 Modifikationen

Hier werden die Abweichungen zur originalen HC1 Vorlage beschrieben.

**ledWait** Das im Blockdiagramm 1 zu sehende Signal *ledWait* wurde von mir hinzugefügt und ist nicht Bestandteil des ursprünglichen HC1 Rechners. Es dient zur Darstellung einer Eingabeaufforderung.

## 2 Entities

### 2.1 Accumulator

 


Abbildung 4: Accumulator - Block

#### 2.1.1 Ports

Name	Type	Bitlength	Direction
clk	std_logic	1	Input
accLoad	std_logic	1	Input
accSel	std_logic_vector	2	Input
keyIn	std_logic_vector	8	Input
memOut	std_logic_vector	8	Input
aluOut	std_logic_vector	8	Input
accOut	std_logic_vector	8	Output
posFlag	std_logic	1	Output
zeroFlag	std_logic	1	Output

Tabelle 2: Accumulator Ports



## 2.2 Arithmetic Logical Unit

 


Abbildung 5: Arithmetic Logical Unit - Block

*Dies ist der einzige Baustein des HC1 ohne Taktsignal.*

### 2.2.1 Ports

Name	Type	Bitlength	Direction
aluOp	std_logic_vector	2	Input
memOut	std_logic_vector	8	Input
accOut	std_logic_vector	8	Input
aluOut	std_logic_vector	8	Output

Tabelle 3: Arithmetic Logical Unit Ports

## 2.3 Control Unit

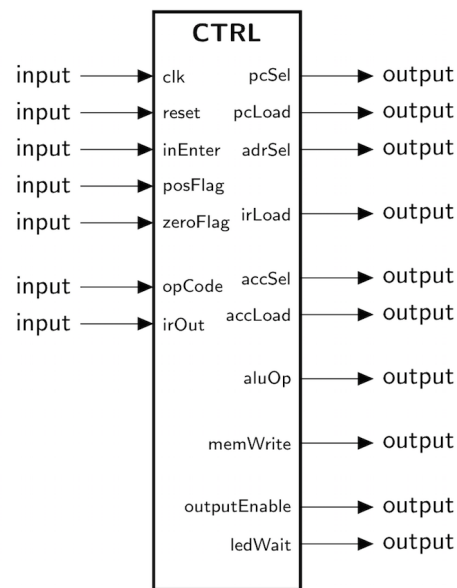


Abbildung 6: Control Unit - Block

Die Control Unit steuert alle Prozesse des Rechners. Sie besteht aus einer State Machine welche die Eingangssignale auswertet und darauf basierend die Ausgänge setzt.

### 2.3.1 Ports

Name	Type	Bitlength	Direction
clk	std_logic	1	Input
reset	std_logic	1	Input
inEnter	std_logic	1	Input
posFlag	std_logic	1	Input
zeroFlag	std_logic	1	Input
opCode	std_logic_vector	3	Input
irOut	std_logic_vector	5	Input

Tabelle 4: Control Unit Input Ports

Wie am Ende des Architekturkapitels 1.4 erklärt ist das *ledWait* Signal nicht Bestandteil des ursprünglichen HC1 Rechners.

### 2.3.2 State Machine

Im folgenden ein Beispiel wie die State Machine der Control Unit aussehen kann:

Name	Type	Bitlength	Direction
pcSel	std_logic_vector	1	Output
pcLoad	std_logic	1	Output
adrSel	std_logic	1	Output
irLoad	std_logic	1	Output
accSel	std_logic_vector	2	Output
accLoad	std_logic	1	Output
aluOp	std_logic_vector	2	Output
memWrite	std_logic	1	Output
outputEnable	std_logic	1	Output
ledWait (optional)	std_logic	1	Output

Tabelle 5: Control Unit Output Ports

 


Abbildung 7: Control Unit - State Machine

Da die Abbildung etwas komplex wirkt ist hier nochmals der VHDL Code zum Erstellen eines solchen State Machine Typen abgebildet.

```

1  type state_type is (
2      RESET_STATE,                -- Reset CPU
3
4      CTRL_LOAD_IR,              -- New Instruction from IR
5
6      MEM_STORE,                 -- Write Memory
7      ACC_MEM,                  -- Acc load Memory
8
9      ACC_ALU_ADD,               -- Acc load ALU with ALU-Add Operation
10     ACC_ALU_SUB,               -- Acc load ALU with ALU-Sub Operation
11     ACC_ALU_NAND,             -- Acc load ALU with ALU-Nand Operation
12

```

```

13      ACC_inEnter,                -- Acc load key_in when inEnter is set
14
15      JUMP_PC_MEM,               -- PC Jump to Address in Memory
16
17      NOP_PC,                   -- Update PC
18      NOP_OUT,                  -- Enable Output while not inEnter
19      NOP_MEM,                  -- Update MEM
20      NOP_IR                    -- Update IR
21 );

```

### 2.3.3 Implementationshinweis

Es gibt verschiedene Wege das Control Unit Verhalten in VHDL zu implementieren. Das Hauptproblem hierbei ist es einen Weg zu finden die Control Unit taktgesteuert zu implementieren ohne *inferred latches* zu generieren.

Ein Weg dies zu tun ist folgender. Zuerst werden drei verschiedene Prozesse definiert:

1. Eingangssignale State Prozess - **Asynchroner Prozess**
2. Takt Prozess - **Taktsynchroner Prozess**
3. State Ausgangssignal Prozess - **Taktsynchroner Prozess**

**Eingangssignale State Prozess** Dieser Prozess ist sensitiv gegenüber allen Eingangssignalen mit Ausnahme der *clk* und des *reset* Signals.

Der Prozess überprüft beim Aufrufen den aktuellen State und speichert basierend auf den Eingangssignalen den nächsten State in einem internen Signal.

*Um inferred latches zu vermeiden muss der interne nächste State am Anfang des Prozesses auf den aktuellen State gesetzt werden.*

**Takt Prozess** Dieser Prozess aktualisiert den aktuellen State. Hierbei wird der aktuelle State durch den intern gespeicherten State überschrieben.

Zudem wird hier auch das *reset* Signal überprüft.

Die Sensitivitylist enthält das *clk* und das *reset* Signal.

**State Ausgangssignal Prozess** Hier werden alle Ausgangssignale gesetzt. Das einzige Signal in der Sensitivitylist des Prozesses ist das aktuelle State Signal.

Wichtig ist zu verstehen, dass dieser Prozess nur nach dem Takt Prozess aufgerufen wird, da nur dort das State Signal gesetzt wird.

## 2.4 Instruction Register

 


Abbildung 8: Instruction Register - Block

Das Instruction Register splittet den aktuellen Speicherwert (memOut) in einen Befehlscode (opCode) und eine Adresse (irOut).

Das Instruction Register aktualisiert diese Werte nur bei steigender Taktflanke und aktivem irLoad Signal.

### 2.4.1 Ports

Name	Type	Bitlength	Direction
clk	std_logic	1	Input
irLoad	std_logic	1	Input
memOut	std_logic_vector	8	Input
opCode	std_logic_vector	3	Output
irOut	std_logic_vector	5	Output

Tabelle 6: Instruction Register Ports

## 2.5 Memory Unit

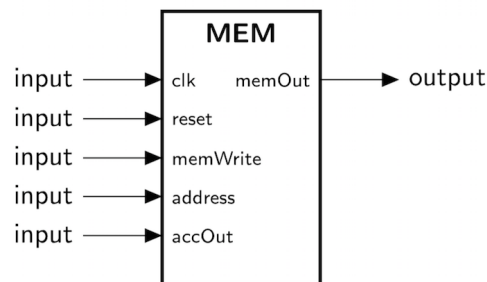


Abbildung 9: Memory Unit - Block

Die Memory Unit stellt den Hauptspeicher des Rechners. Dieser ist 32 Byte groß. Der Speicher wird sowohl für Programmcode als auch für gespeicherte Daten verwendet.

### Funktionsweise:

Das address Eingangssignal setzt die aktuell ausgewählte Speicherstelle. Der dort gespeicherte Wert liegt danach am Ausgangsbus memOut an. Falls der Eingang memWrite gesetzt ist wird der Akkumulatorwert accOut in die gewählte Speicheradresse geschrieben.

Alle Daten werden erst bei einer steigenden Taktflanke.

### Reset:

Über das reset Signal kann der Hauptspeicher zurückgesetzt werden. Hierbei werden normalerweise alle Speicherstellen auf 0 gesetzt.

Zum Testen des Rechners kann hier jedoch auch ein Programm in den Speicher geladen werden.

### 2.5.1 Ports

Name	Type	Bitlength	Direction
clk	std_logic	1	Input

Tabelle 7: Memory Unit Ports

## 2.6 Program Counter

 


Abbildung 10: Program Counter - Block

Der Program Counter hält die aktuelle Speicheradressennummer. Des weiteren erhöht er diese nach bearbeiten jedes Befehls. Er kann zudem für Sprunganweisungen und das Laden von Daten direkt auf einen Wert gesetzt werden.

### 2.6.1 Ports

Name	Type	Bitlength	Direction
clk	std_logic	1	Input

Tabelle 8: Program Counter Ports



## 2.7 Central Processing Unit

 


Abbildung 11: Central Processing Unit - Block

Diese VHDL Entität dient zur Verbindung der anderen Bausteine mittels dem sogenannten *mapping*.

### 2.7.1 Ports

Name	Type	Bitlength	Direction
clk	std_logic	1	Input

Tabelle 9: Central Processing Unit Ports

### 2.7.2 Mapping

## 2.8 Cyclone II Pin Mapping - HC1

Um nun die HC1 CPU mit dem Quartus Board zu benutzen, müssen die Pins des Boards mit den Ein- und Ausgängen der CPU Entität verbunden werden. Dies geschieht mittels einer Top Level Entität.

## A Appendix

### A.1 Accumulator - VHDL

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity accumulator is
5      port(
6          -- Control Input --
7          clk          : in  std_logic;
8          accLoad       : in  std_logic;
9          accSel        : in  std_logic_vector(1 downto 0);
10         -- Data Input --
11         keyIn         : in  std_logic_vector(7 downto 0);
12         memOut        : in  std_logic_vector(7 downto 0);
13         aluOut        : in  std_logic_vector(7 downto 0);
14         -- Data Output --
15         accOut        : out std_logic_vector(7 downto 0);
16         posFlag       : out std_logic;
17         zeroFlag      : out std_logic
18     );
19 end accumulator;
20
21 architecture rtl of accumulator is
22
23     -- Register to hold the output
24     signal holdAccOut : std_logic_vector(7 downto 0);
25
26 begin
27     CLK_PROCESS : process(clk)
28     begin
29         if rising_edge(clk) then
30             -- Load new input
31             if accLoad = '1' then
32                 if accSel = "00" then          -- Load ALU
33                     holdAccOut <= aluOut;
34                 elsif accSel = "01" then      -- Load Memory
35                     holdAccOut <= memOut;
36                 elsif accSel = "10" then      -- Load Keyinput
37                     holdAccOut <= keyIn;
38                 else                          -- Not used Value
39                     holdAccOut <= "00000000";
40                 end if;
41             end if;
42

```

```
43         -- Set Zero Flag
44         if holdAccOut = "00000000" then
45             zeroFlag <= '1';
46         else
47             zeroFlag <= '0';
48         end if;
49         -- Set Positive Flag
50         if holdAccOut(7) = '0' then
51             posFlag <= '1';
52         else
53             posFlag <= '0';
54         end if;
55
56         -- Set Output
57         accOut <= holdAccOut;
58     end if;
59 end process;
60
61 end;
```

## A.2 Arithmetic Logical Unit - VHDL

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity arithmetic_logic_unit is
6      port(
7          -- Control Input --
8          aluOp      : in  std_logic_vector(1 downto 0);
9          -- Data Input --
10         memOut      : in  std_logic_vector(7 downto 0);
11         accOut      : in  std_logic_vector(7 downto 0);
12         -- Data Output --
13         aluOut      : out std_logic_vector(7 downto 0)
14     );
15 end arithmetic_logic_unit;
16
17 architecture rtl of arithmetic_logic_unit is
18 begin
19
20     -- Set output based on aluOp
21     with aluOp select aluOut <=
22         std_logic_vector(signed(memOut) + signed(accOut)) when "00",    -- ADD
23         std_logic_vector(signed(memOut) - signed(accOut)) when "01",    -- SUB
24         not (memOut and accOut) when "10",                               -- NAND
25         "00000000" when others;                                         -- Not used operation
26
27 end;
```

### A.3 Control Unit - VHDL

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity control_unit is
5      port(
6          -- Control Input --
7          clk          : in  std_logic;
8          reset        : in  std_logic;
9          inEnter      : in  std_logic;
10         posFlag      : in  std_logic;
11         zeroFlag     : in  std_logic;
12
13         -- Data Input --
14         opCode       : in  std_logic_vector(2 downto 0);
15         irOut        : in  std_logic_vector(4 downto 0);
16
17         -- Program Counter Output --
18         pcSel        : out std_logic_vector(1 downto 0);
19         pcLoad       : out std_logic;
20         adrSel       : out std_logic;
21
22         -- Instruction Register Output --
23         irLoad       : out std_logic;
24
25         -- Accumulator Output --
26         accSel       : out std_logic_vector(1 downto 0);
27         accLoad      : out std_logic;
28
29         -- Arithmetic Logic Unit Output --
30         aluOp        : out std_logic_vector(1 downto 0);
31
32         -- Memory Output --
33         memWrite     : out std_logic;
34
35         -- Generic Output --
36         outputEnable : out std_logic;
37         ledWait      : out std_logic
38     );
39 end control_unit;
40
41 -----
42 -- Control Flow --
43 -----

```

```

44  --                                     --
45  -- 1. state      <- nextState on clock    --
46  -- 2. output    <- based on state        --
47  -- 3.           repeat 1 & 2             --
48  --                                     --
49  -- x. nextState  <- when input gets changed --
50  -- -----
51
52  architecture rtl of control_unit is
53      type state_type is (
54          RESET_STATE,          -- Reset CPU
55
56          CTRL_LOAD_IR,         -- New Instruction from IR
57
58          MEM_STORE,            -- Write Memory
59          ACC_MEM,              -- Acc load Memory
60
61          ACC_ALU_ADD,          -- Acc load ALU with ALU-Add Operation
62          ACC_ALU_SUB,          -- Acc load ALU with ALU-Sub Operation
63          ACC_ALU_NAND,         -- Acc load ALU with ALU-Nand Operation
64
65          ACC_inEnter,          -- Acc load key_in when inEnter is set
66
67          JUMP_PC_MEM,          -- PC Jump to Address in Memory
68
69          NOP_PC,               -- Update PC
70          NOP_OUT,              -- Enable Output while not inEnter
71          NOP_MEM,              -- Update MEM
72          NOP_IR                -- Update IR
73      );
74      signal state              : state_type := RESET_STATE;
75      signal nextState          : state_type := RESET_STATE;
76
77  begin
78      CLOCK_PROCESS : process(clk, reset)
79      begin
80          if reset = '1' then
81              state <= RESET_STATE;
82          elsif rising_edge(clk) then
83              state <= nextState;
84          end if;
85      end process;
86
87      -- This process updates the next state based on the incoming signals
88      --

```

```

89     INPUT_STATE_PROCESS : process(state, inEnter, opCode, irOut, zeroFlag, posFlag)
90     begin
91         nextState <= state;      -- prevents inferred latches,
92                                   -- because nextState needs to be set even if
93                                   -- the following case is going to set it
94
95         case (state) is
96
97             -- On reset pc is set to address 0x00 so no nop_pc is needed
98             when RESET_STATE =>
99                 nextState <= NOP_MEM;
100
101             -- Next State depends on inputs
102             when CTRL_LOAD_IR =>
103                 -- Going through opCodes
104                 case (opCode) is
105                     when "000" =>      -- LOAD
106                         nextState <= ACC_MEM;
107                     when "001" =>
108                         nextState <= MEM_STORE;
109                     when "010" =>      -- ADD
110                         nextState <= ACC_ALU_ADD;
111                     when "011" =>      -- SUB
112                         nextState <= ACC_ALU_SUB;
113
114                     when "100" =>      -- NAND, IN, OUT
115                         -- Depends on irOut data
116                         if irOut = "00000" then      -- IN
117                             nextState <= ACC_inEnter;
118                         elsif irOut = "00001" then      -- OUT
119                             nextState <= NOP_OUT;
120                         else      -- NAND
121                             nextState <= ACC_ALU_NAND;
122                         end if;
123
124                     when "101" =>      -- JUMP ZERO
125                         if zeroFlag = '1' then
126                             nextState <= JUMP_PC_MEM;
127                         else
128                             nextState <= NOP_PC;
129                         end if;
130                     when "110" =>      -- JUMP POSITIVE
131                         if posFlag = '1' then
132                             nextState <= JUMP_PC_MEM;
133                         else

```



```

134         nextState <= NOP_PC;
135     end if;
136     when others =>          -- JUMP ALWAYS
137         nextState <= JUMP_PC_MEM;
138 end case;
139
140 when ACC_inEnter | NOP_OUT =>
141     if inEnter = '1' then
142         nextState <= NOP_PC;
143     else
144         nextState <= state;
145     end if;
146
147 when NOP_PC =>
148     nextState <= NOP_MEM;
149     -- JUMP_PC_MEM skips NOP_PC and NOP_MEM
150 when JUMP_PC_MEM | NOP_MEM =>
151     nextState <= NOP_IR;
152 when NOP_IR =>
153     nextState <= CTRL_LOAD_IR;
154
155     -- Next State is always NOP_PC
156 when others =>
157     nextState <= NOP_PC;
158
159 end case;
160 end process;
161
162 -- This process sets the output based on the current state
163 --
164 STATE_OUTPUT_PROCESS : process(state)
165 begin
166     case (state) is
167         when RESET_STATE =>          -- Reset CPU
168             -- PC
169             pcSel      <= "10";
170             pcLoad     <= '1';
171             adrSel     <= '0';
172             -- IR
173             irLoad     <= '0';
174             -- ACC
175             accSel     <= "00";
176             accLoad    <= '0';
177             -- ALU
178             aluOp      <= "00";

```

```

179         -- MEM
180         memWrite      <= '0';
181         -- GEN
182         outputEnable <= '0';
183         ledWait       <= '0';
184
185         when CTRL_LOAD_IR =>           -- New Instruction from IR
186             -- PC
187             pcSel        <= "00";
188             pcLoad       <= '0';
189             adrSel       <= '1';
190             -- IR
191             irLoad       <= '0';
192             -- ACC
193             accSel       <= "00";
194             accLoad      <= '0';
195             -- ALU
196             aluOp        <= "00";
197             -- MEM
198             memWrite     <= '0';
199             -- GEN
200             outputEnable <= '0';
201             ledWait      <= '0';
202
203         when MEM_STORE =>             -- Write Memory In
204             -- PC
205             pcSel        <= "00";
206             pcLoad       <= '0';
207             adrSel       <= '1';
208             -- IR
209             irLoad       <= '0';
210             -- ACC
211             accSel       <= "ZZ";
212             accLoad      <= '0';
213             -- ALU
214             aluOp        <= "00";
215             -- MEM
216             memWrite     <= '1';
217             -- GEN
218             outputEnable <= '0';
219             ledWait      <= '0';
220
221         when ACC_MEM =>               -- Acc load Memory
222             -- PC
223             pcSel        <= "00";

```

```

224         pcLoad      <= '0';
225         adrSel       <= '0';
226         -- IR
227         irLoad       <= '0';
228         -- ACC
229         accSel       <= "01";
230         accLoad      <= '1';
231         -- ALU
232         aluOp        <= "00";
233         -- MEM
234         memWrite     <= '0';
235         -- GEN
236         outputEnable <= '0';
237         ledWait      <= '0';
238
239         when ACC_ALU_ADD =>          -- Acc load ALU with ALU-Add Operation
240             -- PC
241             pcSel      <= "00";
242             pcLoad     <= '0';
243             adrSel     <= '0';
244             -- IR
245             irLoad     <= '0';
246             -- ACC
247             accSel     <= "00";
248             accLoad    <= '1';
249             -- ALU
250             aluOp      <= "00";
251             -- MEM
252             memWrite   <= '0';
253             -- GEN
254             outputEnable <= '0';
255             ledWait    <= '0';
256
257         when ACC_ALU_SUB =>          -- Acc load ALU with ALU-Sub Operation
258             -- PC
259             pcSel      <= "00";
260             pcLoad     <= '0';
261             adrSel     <= '0';
262             -- IR
263             irLoad     <= '0';
264             -- ACC
265             accSel     <= "00";
266             accLoad    <= '1';
267             -- ALU
268             aluOp      <= "01";

```

```

269         -- MEM
270         memWrite      <= '0';
271         -- GEN
272         outputEnable  <= '0';
273         ledWait       <= '0';
274
275         when ACC_ALU_NAND =>           -- Acc load ALU with ALU-Nand Operation
276             -- PC
277             pcSel       <= "00";
278             pcLoad      <= '0';
279             adrSel      <= '0';
280             -- IR
281             irLoad      <= '0';
282             -- ACC
283             accSel      <= "00";
284             accLoad     <= '1';
285             -- ALU
286             aluOp       <= "10";
287             -- MEM
288             memWrite    <= '0';
289             -- GEN
290             outputEnable <= '0';
291             ledWait     <= '0';
292
293         when ACC_inEnter =>           -- Acc load key_in when inEnter
294             -- PC
295             pcSel       <= "00";
296             pcLoad      <= '0';
297             adrSel      <= '0';
298             -- IR
299             irLoad      <= '0';
300             -- ACC
301             accSel      <= "10";
302             accLoad     <= '1';
303             -- ALU
304             aluOp       <= "00";
305             -- MEM
306             memWrite    <= '0';
307             -- GEN
308             outputEnable <= '0';
309             ledWait     <= '1';
310
311         when JUMP_PC_MEM =>           -- PC Jump to Address
312             -- PC
313             pcSel       <= "01";

```

```

314         pcLoad      <= '1';
315         adrSel       <= '1';
316         -- IR
317         irLoad       <= '0';
318         -- ACC
319         accSel       <= "00";
320         accLoad      <= '0';
321         -- ALU
322         aluOp        <= "00";
323         -- MEM
324         memWrite     <= '0';
325         -- GEN
326         outputEnable <= '0';
327         ledWait      <= '0';
328
329         when NOP_PC => -- Update PC
330             -- PC
331             pcSel      <= "00";
332             pcLoad     <= '1';
333             adrSel     <= '0';
334             -- IR
335             irLoad     <= '0';
336             -- ACC
337             accSel     <= "00";
338             accLoad    <= '0';
339             -- ALU
340             aluOp      <= "00";
341             -- MEM
342             memWrite   <= '0';
343             -- GEN
344             outputEnable <= '0';
345             ledWait    <= '0';
346
347         when NOP_OUT => -- Enable Output
348             -- PC
349             pcSel      <= "00";
350             pcLoad     <= '0';
351             adrSel     <= '0';
352             -- IR
353             irLoad     <= '0';
354             -- ACC
355             accSel     <= "00";
356             accLoad    <= '0';
357             -- ALU
358             aluOp      <= "00";

```

```

359         -- MEM
360         memWrite      <= '0';
361         -- GEN
362         -- GEN
363         outputEnable <= '1';
364         ledWait       <= '1';
365
366         when NOP_MEM =>                -- Update MEM
367             -- PC
368             pcSel      <= "00";
369             pcLoad     <= '0';
370             adrSel     <= '0';
371             -- IR
372             irLoad     <= '0';
373             -- ACC
374             accSel     <= "00";
375             accLoad    <= '0';
376             -- ALU
377             aluOp      <= "00";
378             -- MEM
379             memWrite   <= '0';
380             -- GEN
381             outputEnable <= '0';
382             ledWait    <= '0';
383
384         when others =>                -- Update IR (NOP_IR)
385             -- PC
386             pcSel      <= "00";
387             pcLoad     <= '0';
388             adrSel     <= '0';
389             -- IR
390             irLoad     <= '1';
391             -- ACC
392             accSel     <= "00";
393             accLoad    <= '0';
394             -- ALU
395             aluOp      <= "00";
396             -- MEM
397             memWrite   <= '0';
398             -- GEN
399             outputEnable <= '0';
400             ledWait    <= '0';
401         end case;
402     end process;
403

```

404    **end;**

## A.4 Instruction Register - VHDL

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity instruction_register is
5      port(
6          clk      : in  std_logic;
7          irLoad   : in  std_logic;
8          memOut   : in  std_logic_vector(7 downto 0);
9          opCode   : out std_logic_vector(2 downto 0);
10         irOut    : out std_logic_vector(4 downto 0)
11     );
12 end instruction_register;
13
14 architecture rtl of instruction_register is
15 begin
16
17     -- Simple memory signal splitter. On clock signal set op_code and ir_out
18     -- (memory address) from memory output
19     --
20     CLK_PROCESS : process(clk)
21     begin
22         if rising_edge(clk) then
23             if irLoad = '1' then
24                 opCode <= memOut(7 downto 5);
25                 irOut  <= memOut(4 downto 0);
26             end if;
27         end if;
28     end process;
29
30 end;
```



## A.5 Memory Unit - VHDL

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity memory_unit is
6      port(
7          -- Control Input --
8          clk          : in  std_logic;
9          reset        : in  std_logic;
10         memWrite     : in  std_logic;
11         -- Data Input --
12         address      : in  std_logic_vector(4 downto 0);
13         accOut       : in  std_logic_vector(7 downto 0);
14         -- Data Output --
15         memOut       : out std_logic_vector(7 downto 0)
16     );
17 end memory_unit;
18
19 architecture rtl of memory_unit is
20     type ram_type is array (31 downto 0) of std_logic_vector(7 downto 0);
21
22     signal ram          : ram_type;
23
24     -- holds output address until next clk
25     signal readAddress  : std_logic_vector(4 downto 0);
26
27 begin
28     RAM_PROCESS : process(clk, reset)
29     begin
30         if reset = '1' then
31             -- Default Code
32
33             -- Some Values
34             ram(31) <= "00000110";    -- Value: 0x06
35             ram(30) <= "00000101";    -- Value: 0x05
36             ram(29) <= "00000100";    -- Value: 0x04
37             ram(28) <= "00000011";    -- Value: 0x03
38             ram(27) <= "00000010";    -- Value: 0x02
39             ram(26) <= "00000001";    -- Value: 0x01
40             ram(25) <= "00000000";    -- Value: 0x00
41
42             -- Default Program (Instruction Testing)
43             --

```

```

44      --      Ins  /  Addr
45      ram(00) <= "000" & "11001"; -- ACC <- 0x00
46      ram(01) <= "100" & "00000"; -- ACC <- IN
47      ram(02) <= "001" & "11000"; -- MEM(24) <- ACC
48      ram(03) <= "100" & "00000"; -- ACC <- IN
49      ram(04) <= "001" & "10111"; -- MEM(23) <- ACC
50      -- ADD
51      ram(05) <= "010" & "11000"; -- ACC <- ACC + MEM(24)
52      ram(06) <= "100" & "00001"; -- OUT <- ACC
53      -- SUB
54      ram(07) <= "000" & "11000"; -- ACC <- MEM(24)
55      ram(08) <= "011" & "10111"; -- ACC <- ACC - MEM(23)
56      ram(09) <= "100" & "00001"; -- OUT <- ACC
57      -- NAND
58      ram(10) <= "000" & "11000"; -- ACC <- MEM(24)
59      ram(11) <= "100" & "10111"; -- ACC <- ACC nand MEM(23)
60      ram(12) <= "100" & "00001"; -- OUT <- ACC
61      -- JPos
62      ram(13) <= "000" & "11111"; -- ACC <- MEM(31)
63      ram(14) <= "110" & "10010"; -- PC <- 18
64      -- JZ
65      ram(18) <= "000" & "11001"; -- ACC <- MEM(25)
66      ram(19) <= "101" & "10000"; -- PC <- 16
67      -- Jump
68      ram(15) <= "100" & "00001"; -- OUT <- ACC
69      ram(16) <= "111" & "00000"; -- PC <- 00
70
71      elsif rising_edge(clk) then
72          -- Write data to memory
73          if memWrite = '1' then
74              ram(to_integer(unsigned(address))) <= accOut;
75          end if;
76          -- Store output adress
77          readAddress <= address;
78      end if;
79  end process;
80
81      -- Set output (updates on RAM_PROCESS through readAddress signal)
82      memOut <= ram(to_integer(unsigned(readAddress)));
83
84  end;
```

## A.6 Program Counter - VHDL

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity program_counter is
6      port(
7          -- Control Input --
8          clk          : in  std_logic;
9          pcLoad       : in  std_logic;
10         pcSel        : in  std_logic_vector(1 downto 0);
11         adrSel       : in  std_logic;
12         -- Data Input --
13         irOut        : in  std_logic_vector(4 downto 0);
14         -- Data Output --
15         address      : out std_logic_vector(4 downto 0)
16     );
17 end program_counter;
18
19 architecture rtl of program_counter is
20
21     -- internal pc address
22     signal holdAddress : std_logic_vector(4 downto 0);
23
24 begin
25     PC_PROCESS : process(clk)
26     begin
27         if rising_edge(clk) then
28             if pcLoad = '1' then
29                 if pcSel = "00" then          -- increment counter
30                     holdAddress <= std_logic_vector(unsigned(holdAddress) + 1);
31                 elsif pcSel = "01" then      -- set counter to new address from IR
32                     holdAddress <= irOut;
33                 else                          -- reset counter
34                     holdAddress <= "00000";
35                 end if;
36             end if;
37         end if;
38     end process;
39
40     -- Set output based on adrSel
41     with adrSel select address <=
42         holdAddress when '0',                -- PC address
43         irOut when others;                  -- IR address

```

44

45 `end;`

## A.7 CPU - VHDL

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use work.all;
4
5  entity cpu is
6      port(
7          clk          : in  std_logic;          -- Clock input
8          reset        : in  std_logic;          -- Reset input
9
10         inEnter       : in  std_logic;          -- Enter key
11         keyIn         : in  std_logic_vector(7 downto 0); -- Value input
12
13         ledWait       : out std_logic;          -- Wait for enter
14         ledOut        : out std_logic_vector(7 downto 0); -- Value output
15
16         resetOut      : out std_logic;          -- Reset indicator
17         clkOut        : out std_logic          -- Clock indicator
18     );
19 end cpu;
20
21 architecture rtl of cpu is
22     -- Data Wires
23     signal address : std_logic_vector(4 downto 0); -- PC to MEM
24     signal memOut  : std_logic_vector(7 downto 0); -- MEM to IR, ALU & ACC
25     signal accOut  : std_logic_vector(7 downto 0); -- ACC to MEM, ALU & OUT_LEDS
26     signal opCode  : std_logic_vector(2 downto 0); -- IR to CTRL
27     signal irOut   : std_logic_vector(4 downto 0); -- IR to CTRL & PC
28     signal aluOut  : std_logic_vector(7 downto 0); -- ALU to ACC
29
30     -- Control Wires
31     signal pcSel   : std_logic_vector(1 downto 0); -- PC input address selection
32     signal pcLoad  : std_logic;                    -- PC enable
33     signal adrSel  : std_logic;                    -- PC output address selection
34
35     signal irLoad  : std_logic;                    -- IR enable
36
37     signal accSel  : std_logic_vector(1 downto 0); -- ACC input data selection
38     signal accLoad : std_logic;                    -- ACC enable
39     signal posFlag : std_logic;                    -- ACC data is positive flag
40     signal zeroFlag : std_logic;                   -- ACC data is zero flag
41
42     signal aluOp   : std_logic_vector(1 downto 0); -- ALU operation selection
43     signal memWrite : std_logic;                   -- MEM write enable

```

```
44     signal outputEnable : std_logic;           -- LED output enable
45
46 begin
47
48     -- The following commands connecting the signals, inputs & outputs between
49     -- all single components of the cpu
50     --
51     CTRL : control_unit port map(clk, reset, inEnter, posFlag, zeroFlag, opCode,
52                                   irOut, pcSel, pcLoad, adrSel, irLoad, accSel,
53                                   accLoad, aluOp, memWrite, outputEnable, ledWait);
54     MEM  : memory_unit port map(clk, reset, memWrite, address, accOut, memOut);
55     ALU  : arithmetic_logic_unit port map(aluOp, memOut, accOut, aluOut);
56     ACC  : accumulator port map(clk, accLoad, accSel, keyIn, memOut, aluOut,
57                                   accOut, posFlag, zeroFlag);
58     IR   : instruction_register port map(clk, irLoad, memOut, opCode, irOut);
59     PC   : program_counter port map(clk, pcLoad, pcSel, adrSel, irOut, address);
60
61     -- Setting the value output if output is enabled
62     --
63     ledOut(0) <= accOut(0) and outputEnable;
64     ledOut(1) <= accOut(1) and outputEnable;
65     ledOut(2) <= accOut(2) and outputEnable;
66     ledOut(3) <= accOut(3) and outputEnable;
67
68     ledOut(4) <= accOut(4) and outputEnable;
69     ledOut(5) <= accOut(5) and outputEnable;
70     ledOut(6) <= accOut(6) and outputEnable;
71     ledOut(7) <= accOut(7) and outputEnable;
72
73     -- Setting the clock and reset indicators (added for debugging)
74     --
75     resetOut <= reset;
76     clkOut <= clk;
77
78 end;
```